

Electric Circuits Lab

Teacher : Behnaz Keshavarz Mohammadi
Student : Reyhan Sahraei, Ramtin Kosari

Review of Thevenin's Equivalent Circuit Theorem


April 8, 2025

Overview

Here is book of Electric Circuits Lab experiment on page 64 (Book)

Experiment Info

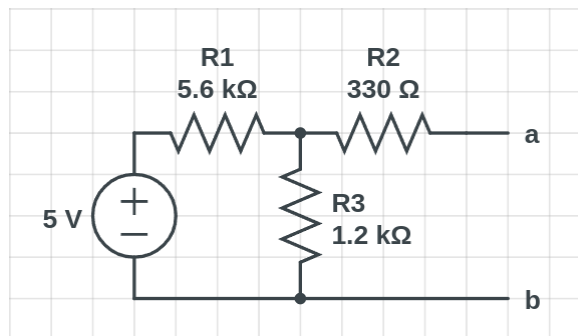- **Purpose** > To verify **Thevenin's Theorem** by determining the Thevenin equivalent voltage and resistance of a given electrical circuit.
- **Necessary Equipment** > Resistors, DC Power, Multimeter, Wires



Steps

1. First we set multimeter on voltage mode
2. Then we measured voltage from a and b and then measured current from there.
3. Then we removed the power source to make resistors form in parallel.

Thevenin Table

$V_{measured}$	$I_{measured}$	R_{th}
0.88V	0.66mA	1333.3 Ω
0.98V	4.5mA	217.8 Ω

